
DC fast charging: vocabulary

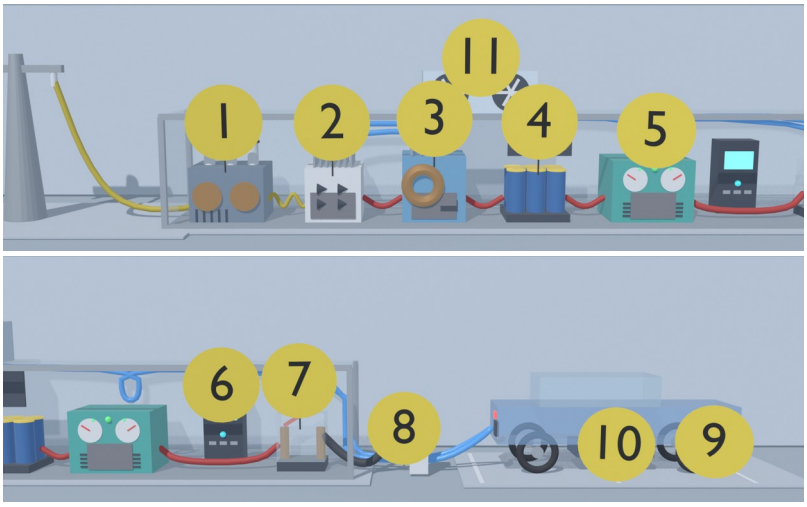Look at the two pictures of the charging station and the car. Each part of the process has a number. Choose the right name from the word box for each number and write it in the table. Then write in your own words what the part does. Every name is used once.




Word box: Contactor • Battery • Rectifier • Cooling system • Transformer • DC/DC converter • Battery management system • PFC stage • Charging cable • DC link capacitor • Charge controller


No.	Name of the part	What does it do?
1		
2		
3		
4		
5		
6		
7		
8		
9		
10		
11		

The seven stations

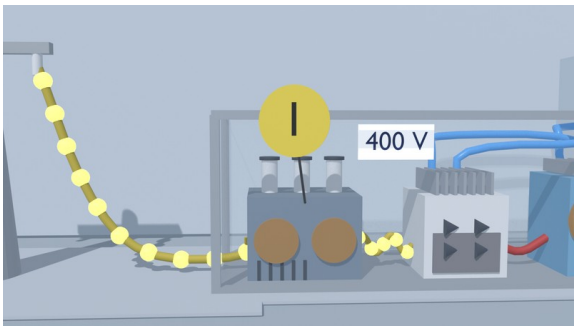
These pictures show where each station of the process takes place. The numbers help you to find the parts.




Station 1 (parts 1)

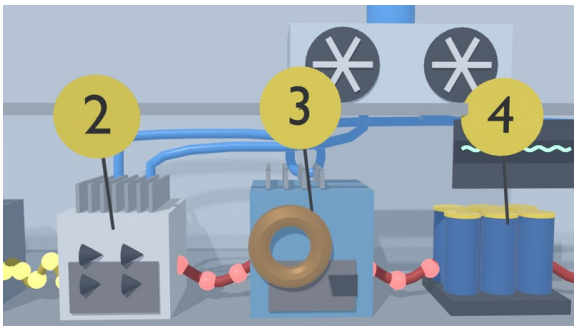


Station 2 (parts 2, 3, 4)

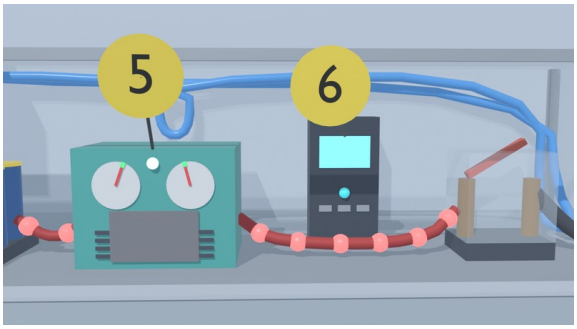


Station 3 (parts 5, 6)

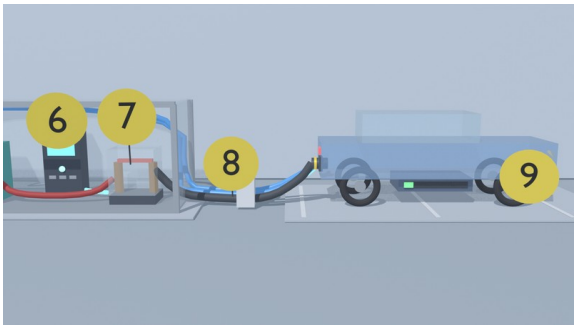


Station 4 (parts 6, 7, 8, 9)

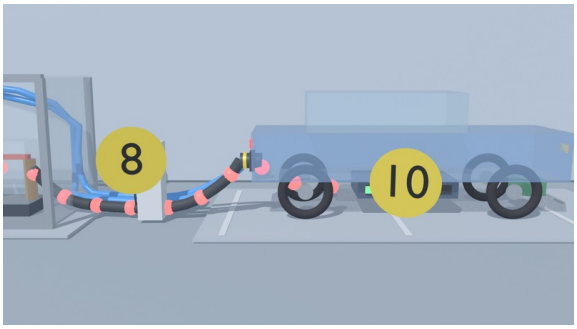

Station 5 (parts 8, 10)

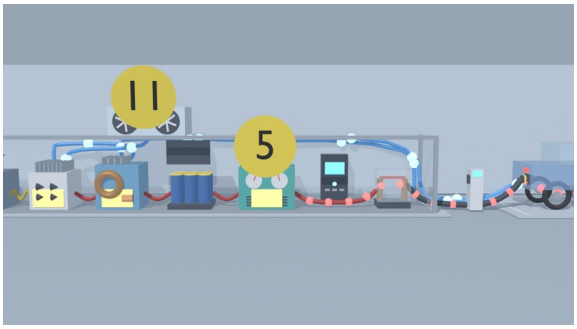

Station 6 (parts 11, 5)

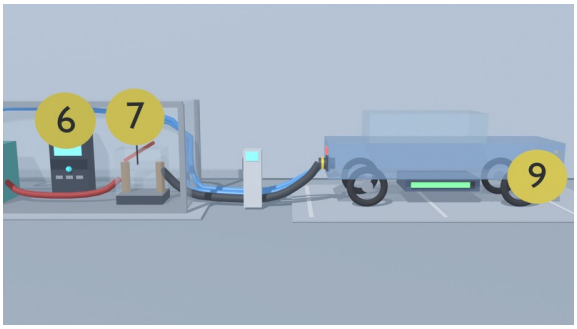

Station 7 (parts 9, 6, 7)